

L26-LB

Reference Design

GNSS Module Series

Rev. L26-LB_Reference_Design_V1.2

Date: 2020-05-14

Status: Released



Our aim is to provide customers with timely and comprehensive service. For any assistance, please contact our company headquarters:

Quectel Wireless Solutions Co., Ltd.

Building 5, Shanghai Business Park Phase III (Area B), No.1016 Tianlin Road, Minhang District, Shanghai 200233, China

Tel: +86 21 5108 6236

Email: info@quectel.com

Or our local office. For more information, please visit:

<http://www.quectel.com/support/sales.htm>

For technical support, or to report documentation errors, please visit:

<http://www.quectel.com/support/technical.htm>

Or email to: support@quectel.com

GENERAL NOTES

QUECTEL OFFERS THE INFORMATION AS A SERVICE TO ITS CUSTOMERS. THE INFORMATION PROVIDED IS BASED UPON CUSTOMERS' REQUIREMENTS. QUECTEL MAKES EVERY EFFORT TO ENSURE THE QUALITY OF THE INFORMATION IT MAKES AVAILABLE. QUECTEL DOES NOT MAKE ANY WARRANTY AS TO THE INFORMATION CONTAINED HEREIN, AND DOES NOT ACCEPT ANY LIABILITY FOR ANY INJURY, LOSS OR DAMAGE OF ANY KIND INCURRED BY USE OF OR RELIANCE UPON THE INFORMATION. ALL INFORMATION SUPPLIED HEREIN IS SUBJECT TO CHANGE WITHOUT PRIOR NOTICE.

COPYRIGHT

THE INFORMATION CONTAINED HERE IS PROPRIETARY TECHNICAL INFORMATION OF QUECTEL WIRELESS SOLUTIONS CO., LTD. TRANSMITTING, REPRODUCTION, DISSEMINATION AND EDITING OF THIS DOCUMENT AS WELL AS UTILIZATION OF THE CONTENT WITHOUT PERMISSION ARE FORBIDDEN. OFFENDERS WILL BE HELD LIABLE FOR PAYMENT OF DAMAGES. ALL RIGHTS ARE RESERVED IN THE EVENT OF A PATENT GRANT OR REGISTRATION OF A UTILITY MODEL OR DESIGN.

Copyright © Quectel Wireless Solutions Co., Ltd. 2020. All rights reserved.

About the Document

Revision History

Version	Date	Author	Description
1.0	2020-03-18	Ronnie HU/ Phil GAO	Initial
1.1	2020-04-29	Ronnie HU	Changed U301 from ADCMP370AKSZ-REEL7 to ADCMP371AKSZ-REEL7.
1.2	2020-05-14	Phil GAO	Updated the recommended value of R301.

Contents

About the Document	2
Contents	3
1 Reference Design.....	4
1.1. Introduction	4
1.2. Schematics	4

1 Reference Design


1.1. Introduction

This document provides the reference design of Quectel L26-LB GNSS module, including the design of power supply, UART and antenna interfaces.

1.2. Schematics

The schematics illustrated in the following pages are provided for your reference only.


Block Diagram

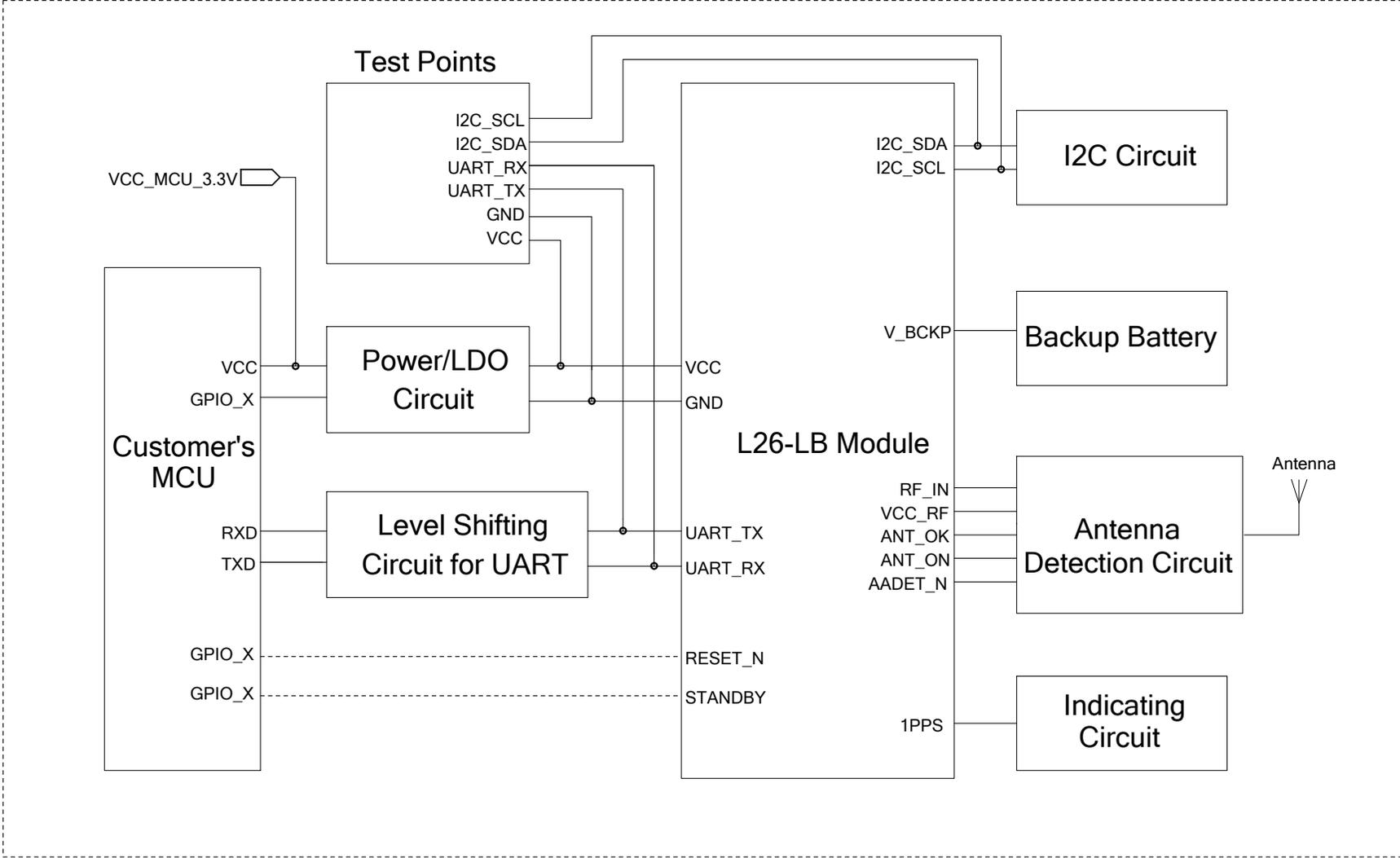


Quectel Wireless Solutions		
DRAWN BY Ronnie HU/Phil GAO	PROJECT L26-LB	TITLE Reference Design
CHECKED BY Storm BAO	SIZE A2	VER 1.2
SHEET 1 / 4		DATE 2020/5/14

3.3V Power Supply and UART Circuits

Customer's MCU

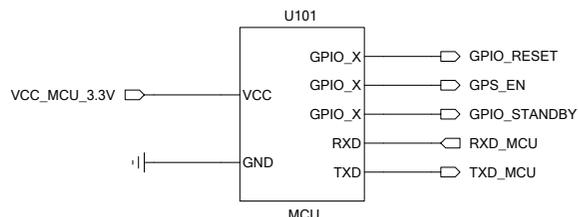

Power Management Circuit (Optional)

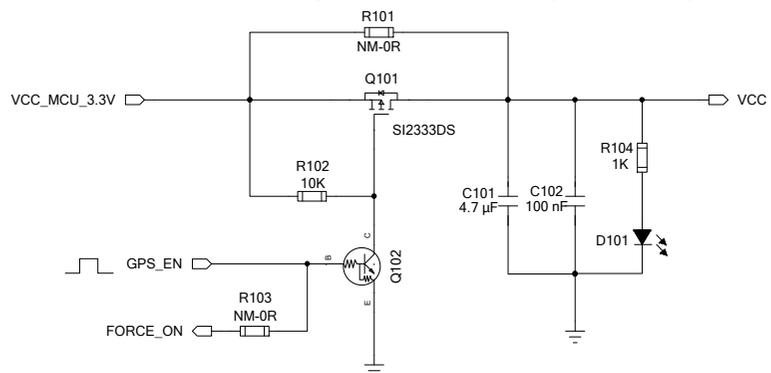


Note:


There are two ways to enter/exit backup mode:

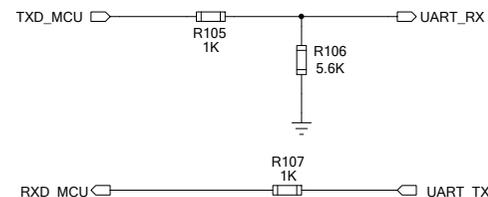1. Sending \$PMTK225,4*2F command makes the module enter backup mode. In such a case, the only way to wake up the module is by pulling FORCE_ON high. In the solution, Q101, Q102 and R102 are not mounted; R101 and R103 are 0 Ω.
2. Cutting off the power supply of VCC while keeping V_BCKP powered, the module will enter backup mode. As soon as the VCC power supply is restored, the module enters full on mode immediately. In the solution, Q101, Q102 and R102 are mounted; R101 and R103 are not mounted.

Level Shifting for UART - Resistor Solution



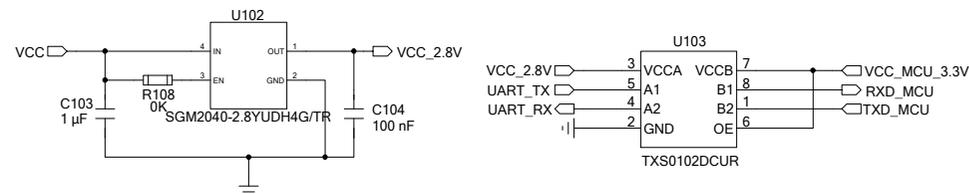Level Shifting for UART - Level Shifter IC Solution



Notes:



1. The above level shifting circuits realize the voltage-level shifting between VCC_MCU_3.3V and 2.8 V (power domain of UART), and block the leakage current from the power-on devices to power-off devices.
2. The level shifter IC solution generally requires VCCA ≤ VCCB, please pay attention to the voltage relationship.

Quectel Wireless Solutions

DRAWN BY Ronnie HU/Phil GAO	PROJECT L26-LB	TITLE Reference Design
CHECKED BY Storm BAO	SIZE A2	VER 1.2
SHEET 2 / 4		DATE 2020/5/14

Module Interfaces

Module Interfaces

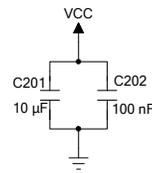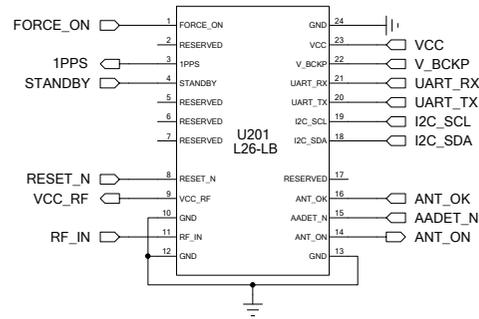


Test Points

- L26_LB_SDA □ I2C_SDA
- L26_LB_SCL □ I2C_SCL
- L26_LB_TXD □ UART_TX
- L26_LB_RXD □ UART_RX
- L26_LB_VCC □ VCC
- GND □ GND

Notes:

1. UART can be used for NMEA sentences output and firmware upgrade.
2. When I2C interface is supported, I2C interface will be used for NMEA sentences output by default.


RTC Backup Power Supply

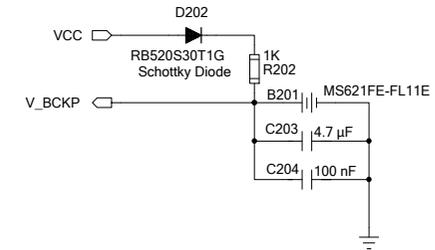

Note:

V_BCKP is designed to supply power for L26-LB RTC logic circuit when VCC is powered off.


I2C Circuit

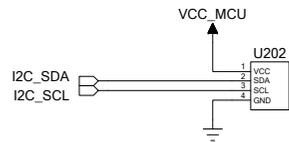

Notes:

1. I2C_SDA/I2C_SCL is pulled up to 2.8 V inside the module.
2. The power domain of I2C is 2.8 V. If the system voltage is not consistent with it, a level shifter circuit must be used.


Indicating Circuit

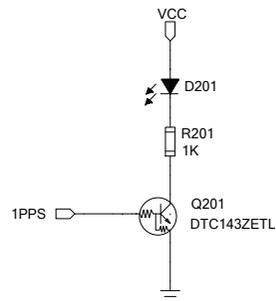

Note:

The 1PPS indicator will blink at 1 Hz frequency after fixing the position.


Reset Circuit

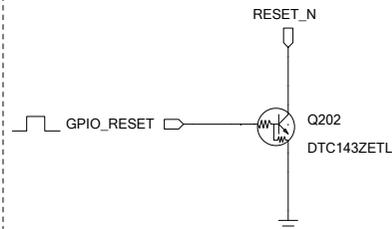

Note:

RESET_N has been pulled up internally.

Standby Circuit

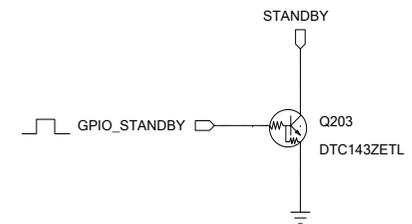

Notes:


1. STANDBY has been pulled up internally.
 2. Enter standby mode: change the STANDBY pin from high to low level.
 3. Exit standby mode: change the STANDBY pin from low to high level.
- For more details, please refer to *Quectel_L26-LB_Hardware_Design*.

Quectel Wireless Solutions

DRAWN BY Ronnie HU/Phil GAO	PROJECT L26-LB	TITLE Reference Design
CHECKED BY Storm BAO	SIZE A2	VER 1.2
SHEET 3 / 4		DATE 2020/5/14

Antenna Interface


Active Antenna

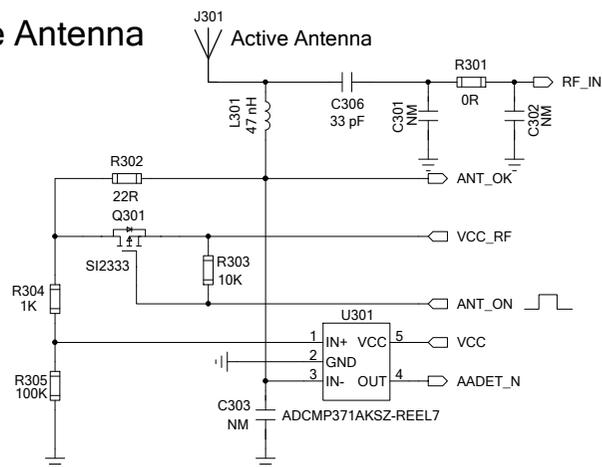

Notes:

- The comparator U301 is used to distinguish the antenna connection status, either normal or open circuit. When ANT_ON is pulled down, the voltage division circuit (R304, R305) divides the voltage of VCC_RF. It is recommended to adjust the value of R304 and R305 appropriately according to the power consumption of active antenna, so as to achieve the following conditions:
When antenna status is open circuit: pin 4 (output) of U301 at low level
When antenna status is normal: pin 4 (output) of U301 at high level
- The R_BIAS (R302) is a must, otherwise the module may be damaged permanently when the antenna is short circuited.
- VCC_RF can be used to supply power for the active antenna. Its voltage range is 2.8 to 4.3 V ($VCC_RF = VCC$), and the typical value is 3.3 V. If VCC_RF cannot meet the antenna's power supply requirements, an external LDO is needed.
- Please keep 50 Ω impedance for RF traces, and keep the trace length as short as possible. For more details, please refer to *Quectel_L26-LB_Hardware_Design*.

Passive Antenna

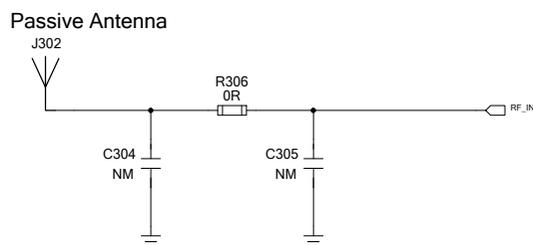

Notes:

- The Π type matching circuit (R306, C304, C305) is reserved for antenna impedance matching. By default, C304 and C305 are not mounted and R306 is 0 Ω .
- Please keep 50 Ω impedance for RF traces, and keep the trace length as short as possible. For more details, please refer to *Quectel_L26-LB_Hardware_Design*.

Quectel Wireless Solutions

DRAWN BY Ronnie HU/Phil GAO	PROJECT L26-LB	TITLE Reference Design
CHECKED BY Storm BAO	SIZE A2	VER 1.2
SHEET 4 / 4		DATE 2020/5/14