

# AG35 Series

# Reference Design

**Automotive Module Series**

Version: 1.1

Date: 2021-05-31

Status: Released



**Our aim is to provide customers with timely and comprehensive service. For any assistance, please contact our company headquarters:**

**Quectel Wireless Solutions Co., Ltd.**

Building 5, Shanghai Business Park Phase III (Area B), No.1016 Tianlin Road, Minhang District, Shanghai 200233, China

Tel: +86 21 5108 6236

Email: [info@quectel.com](mailto:info@quectel.com)

**Or our local office. For more information, please visit:**

<http://www.quectel.com/support/sales.htm>.

**For technical support, or to report documentation errors, please visit:**

<http://www.quectel.com/support/technical.htm>

Or email to [support@quectel.com](mailto:support@quectel.com).

## **General Notes**

Quectel offers the information as a service to its customers. The information provided is based upon customers' requirements. Quectel makes every effort to ensure the quality of the information it makes available. Quectel does not make any warranty as to the information contained herein, and does not accept any liability for any injury, loss or damage of any kind incurred by use of or reliance upon the information. All information supplied herein is subject to change without prior notice.

## **Disclaimer**

While Quectel has made efforts to ensure that the functions and features under development are free from errors, it is possible that these functions and features could contain errors, inaccuracies and omissions. Unless otherwise provided by valid agreement, Quectel makes no warranties of any kind, implied or express, with respect to the use of features and functions under development. To the maximum extent permitted by law, Quectel excludes all liability for any loss or damage suffered in connection with the use of the functions and features under development, regardless of whether such loss or damage may have been foreseeable.

## **Duty of Confidentiality**

The Receiving Party shall keep confidential all documentation and information provided by Quectel, except when the specific permission has been granted by Quectel. The Receiving Party shall not access or use Quectel's documentation and information for any purpose except as expressly provided herein. Furthermore, the Receiving Party shall not disclose any of the Quectel's documentation and information to any third party without the prior written consent by Quectel. For any noncompliance to the above requirements, unauthorized use, or other illegal or malicious use of the documentation and information, Quectel will reserve the right to take legal action.

## Copyright

The information contained here is proprietary technical information of Quectel. Transmitting, reproducing, disseminating and editing this document as well as using the content without permission are forbidden. Offenders will be held liable for payment of damages. All rights are reserved in the event of a patent grant or registration of a utility model or design.

***Copyright © Quectel Wireless Solutions Co., Ltd. 2021. All rights reserved.***

# About the Document

## Revision History

Version	Date	Author	Description
1.0	2017-12-27	Eden LIU	Initial
1.1	2021-05-31	Eden LIU	<ol style="list-style-type: none"> <li>1. Deleted the SGMII interface design.</li> <li>2. Sheet 1: Added the block diagram of AG35 series reference design.</li> <li>3. Sheet 2: Updated the power supply block diagram.</li> <li>4. Sheet 3: Modified the part number of L0101 common mode inductor to DLM11SN900HZ2L; deleted the test point circuit of USB; reserved pin 159; enabled pin 152 (MCLK) and pin 176 (SHDN_N) in U0101-B; updated the name of pins 132–141 in U0101-D for the optional audio function.</li> <li>5. Sheets 3 and 9: Updated the ADC circuit for antenna detection.</li> <li>6. Sheet 4: Removed pins USB_VBUS, USB_D+, USB_D- and USB_ID for U0201, updated the WAKEUP_IN circuit, and added the SHDN_N circuit.</li> <li>7. Sheets 5 and 6: Updated the power supply designs for the AG35 series, AF20, PCM codec, PHY and the SD card interface; added the power supply design for antenna detection.</li> <li>8. Sheet 7: Modified the part number of Q0501–Q0504 to 2SC4617.</li> <li>9. Sheet 8: Optimized the design of reset delay circuit.</li> <li>10. Sheet 9: Optimized the design of antenna interfaces by adding designs for antenna status detection.</li> <li>11. Sheet 10: Updated the exterior trace length requirement of SDIO signal trace to 27 mm.</li> <li>12. Sheet 11: Updated the AF20 antenna circuit, and deleted the pull-up circuit on pin 13 PCM_IN of AF20.</li> </ol>

---

13. Sheet 12: Updated STATUS and USB\_BOOT circuits.

14. Sheet 13: Added the USB interface design.

---

## Contents

About the Document .....	3
Contents .....	5
<b>1 Reference Design</b> .....	<b>6</b>
1.1. Introduction .....	6
1.2. Schematics .....	6

# 1 Reference Design


## 1.1. Introduction

This document provides the reference design for Quectel AG35 series module.

## 1.2. Schematics

The schematics illustrated in the following pages are provided for reference only.

# Block Diagram

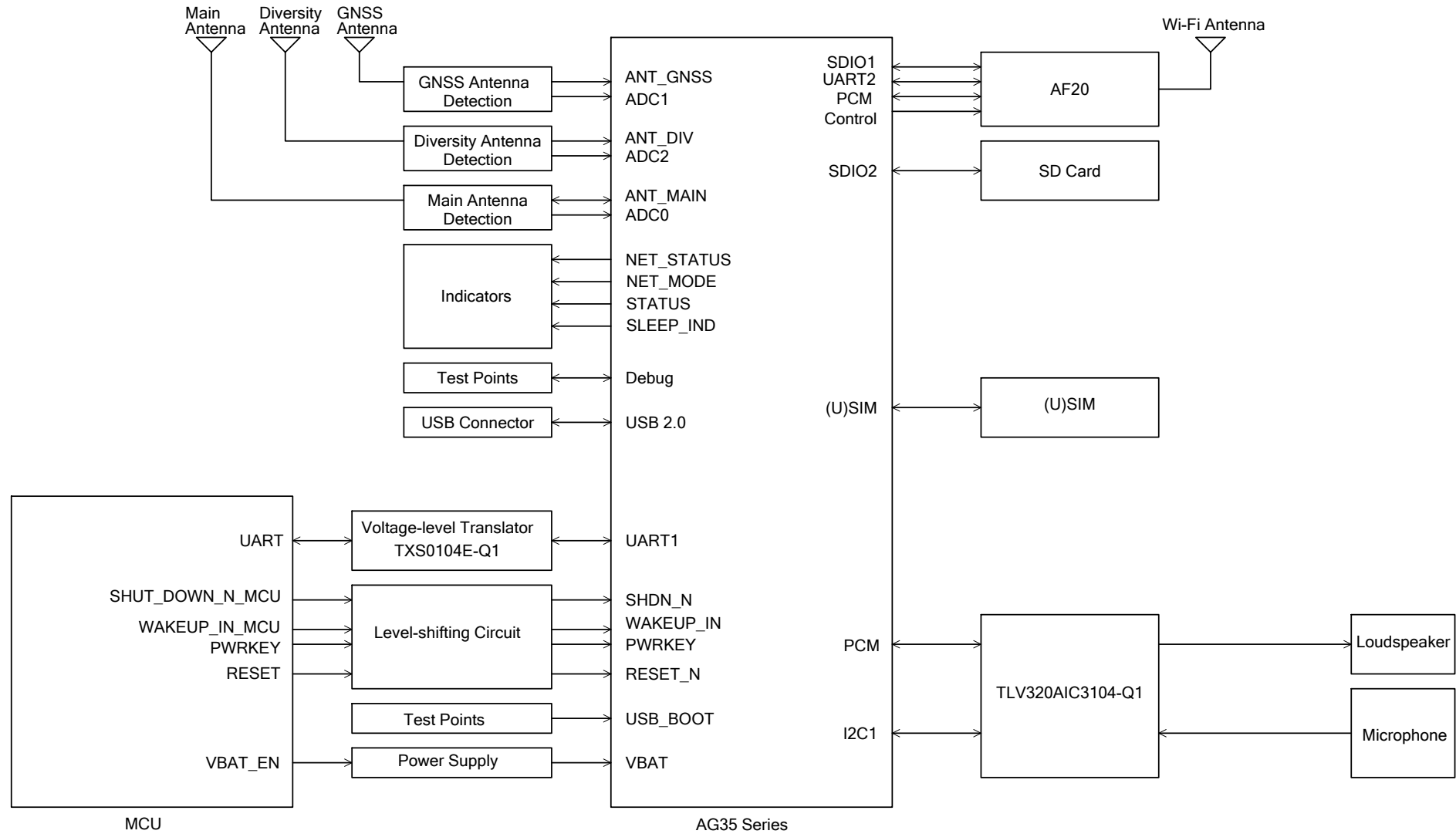

Note:  
Power domain of the MCU is 3.3 V.

Quectel Wireless Solutions		
DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 1 OF 13		DATE 2021/5/31



6

5


4

3

2

1

# Power Supply Block Diagram

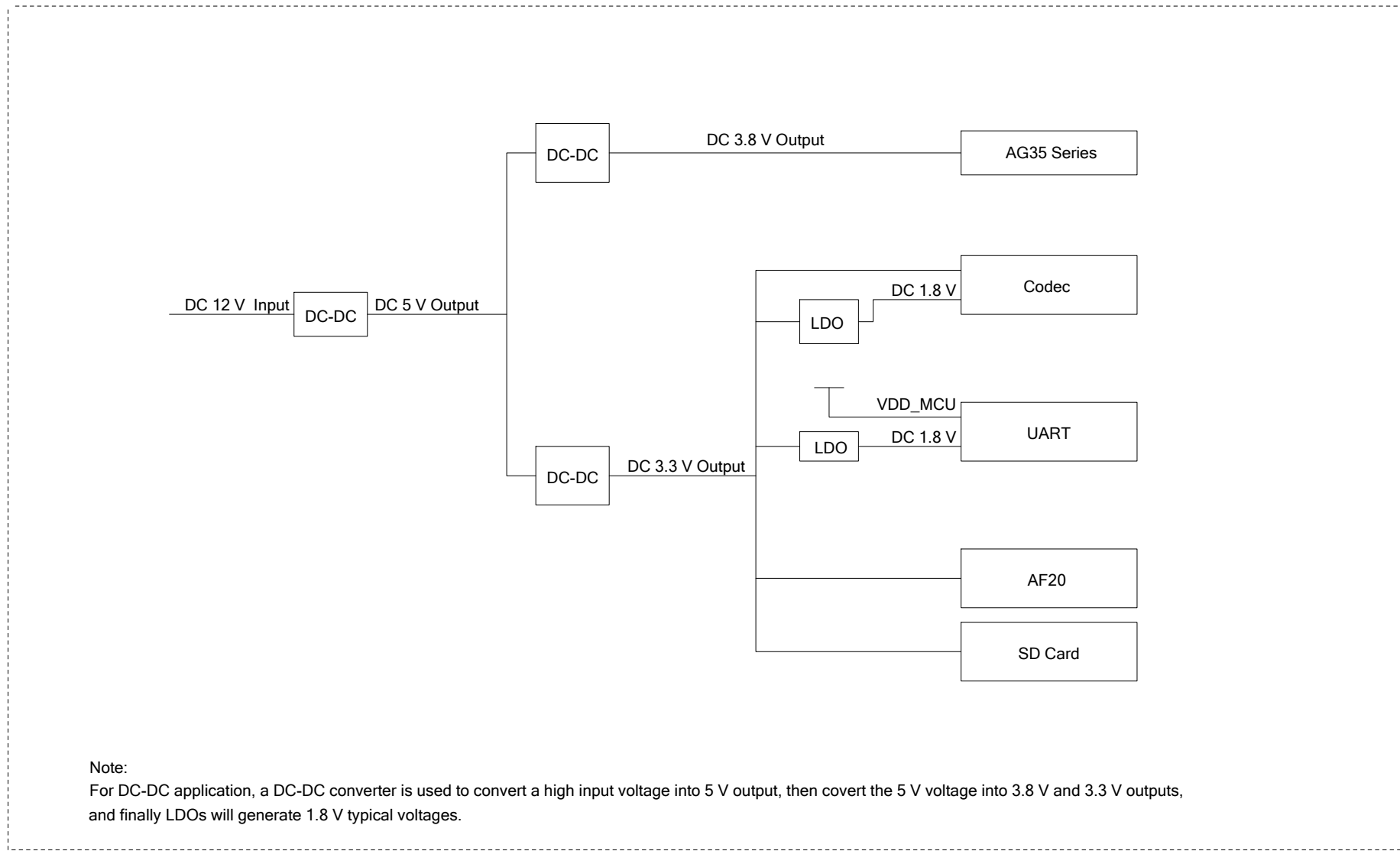

**Note:**  
 For DC-DC application, a DC-DC converter is used to convert a high input voltage into 5 V output, then convert the 5 V voltage into 3.8 V and 3.3 V outputs, and finally LDOs will generate 1.8 V typical voltages.

Quectel Wireless Solutions		
DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 2 OF 13		DATE 2021/5/31

6

5


4

3

2

1

# Module Interface Design

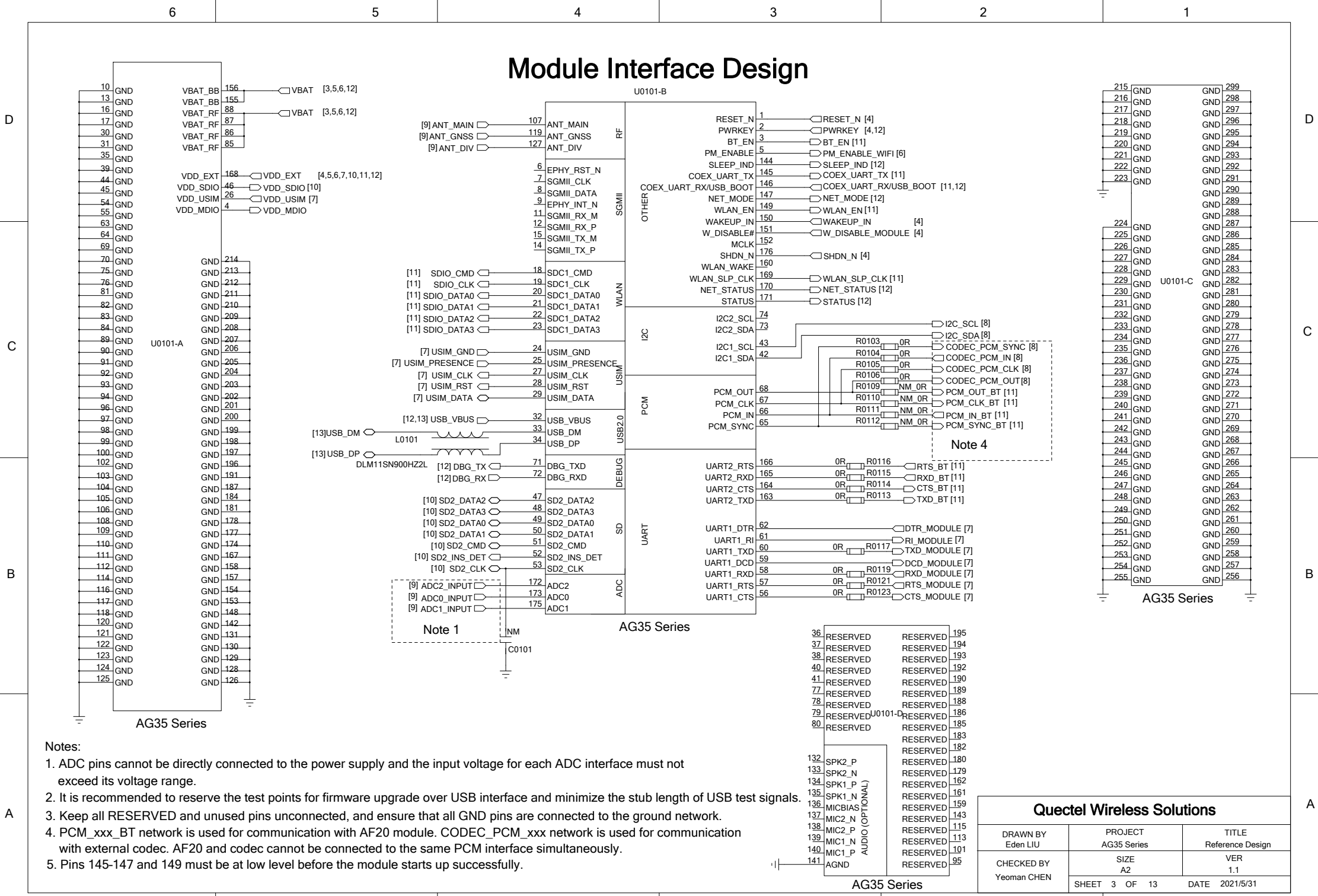








- Notes:
1. ADC pins cannot be directly connected to the power supply and the input voltage for each ADC interface must not exceed its voltage range.
  2. It is recommended to reserve the test points for firmware upgrade over USB interface and minimize the stub length of USB test signals.
  3. Keep all RESERVED and unused pins unconnected, and ensure that all GND pins are connected to the ground network.
  4. PCM\_xxx\_BT network is used for communication with AF20 module. CODEC\_PCM\_xxx network is used for communication with external codec. AF20 and codec cannot be connected to the same PCM interface simultaneously.
  5. Pins 145-147 and 149 must be at low level before the module starts up successfully.

36	RESERVED	RESERVED	195
37	RESERVED	RESERVED	194
38	RESERVED	RESERVED	193
40	RESERVED	RESERVED	192
41	RESERVED	RESERVED	190
77	RESERVED	RESERVED	189
78	RESERVED	RESERVED	188
79	RESERVED	RESERVED	186
80	RESERVED	RESERVED	185
			183
			182
			180
			179
			162
			161
			159
			143
			143
			115
			113
			101
			95

AG35 Series

Quectel Wireless Solutions		
DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 3 OF 13		DATE 2021/5/31

# MCU Interface Design

       


**Notes:**

- U0201 represents the MCU.
- AG35 series module can only work as a USB device and it supports Full Speed and High Speed modes. To communicate through USB interface, MCU needs to support USB host or OTG function. The VBUS pins of MCU and AG35 series module should be powered by a 5 V power system for USB detection, and VBUS\_CTRL is used to turn on/off VBUS power supply. When VBUS\_CTRL is at high level, USB\_VBUS will be powered on.


Quectel Wireless Solutions		
DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 4 OF 13		DATE 2021/5/31

# Power Supply Designs (Part 1)

## Module Power Supply

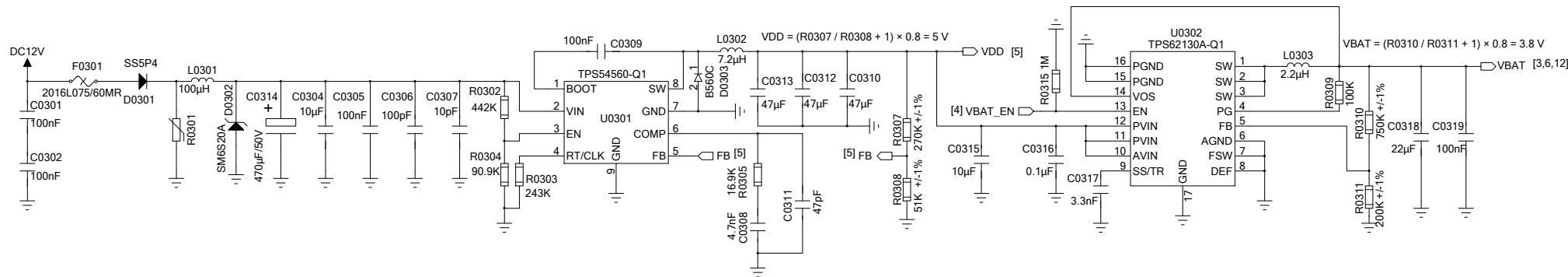

## Codec/PHY/AF20/SD Power Supply

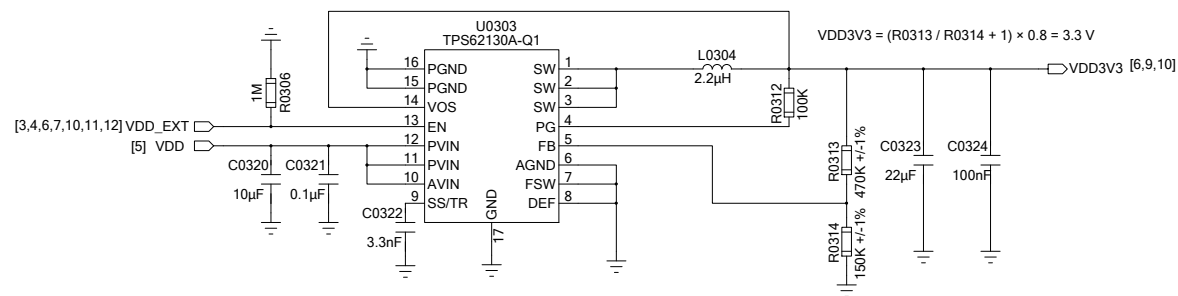

### Notes:


1. The power supply must be able to provide a sufficient current of 3 A at least.
2. VBAT\_EN is used to control power supply of the module. It is at high level by default when the module is in a state of power supply. When VBAT\_EN is at low level, VBAT power supply will be switched off.

### Quectel Wireless Solutions

DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 5 OF 13		DATE 2021/5/31

# Power Supply Designs (Part 2)


## VBAT Design

 

### Notes:

1. The power supply must be able to provide a sufficient current of 2 A at least.
2. VBAT\_BB and VBAT\_RF pins should be routed in star structure.
3. The recommended operating voltage of VBAT is 3.3-4.3 V.
4. The capacitors C0401-C0408 should be placed close to the module's VBAT pins.


## Power Supply for AF20

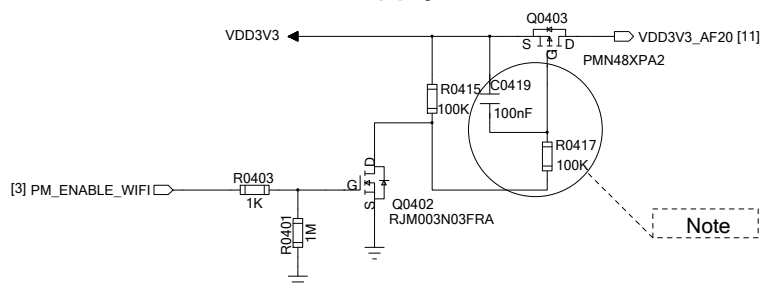


### Note:

The RC circuit, assembled with R0417 and C0419, is used to delay the start-up of MOSFET switch circuit.

## Power Supply for Antenna Detection

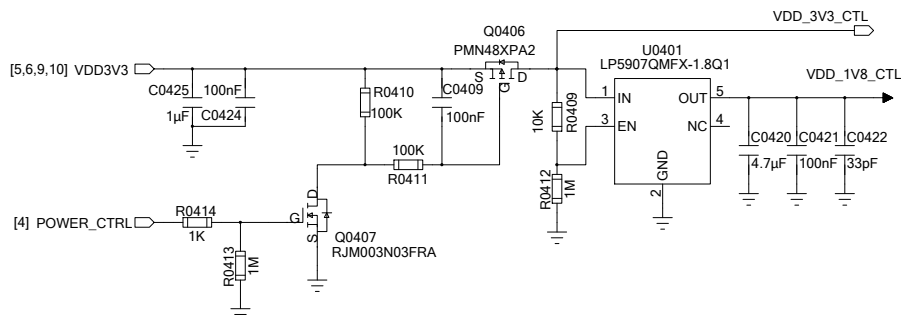

## Power Supply for PCM Codec

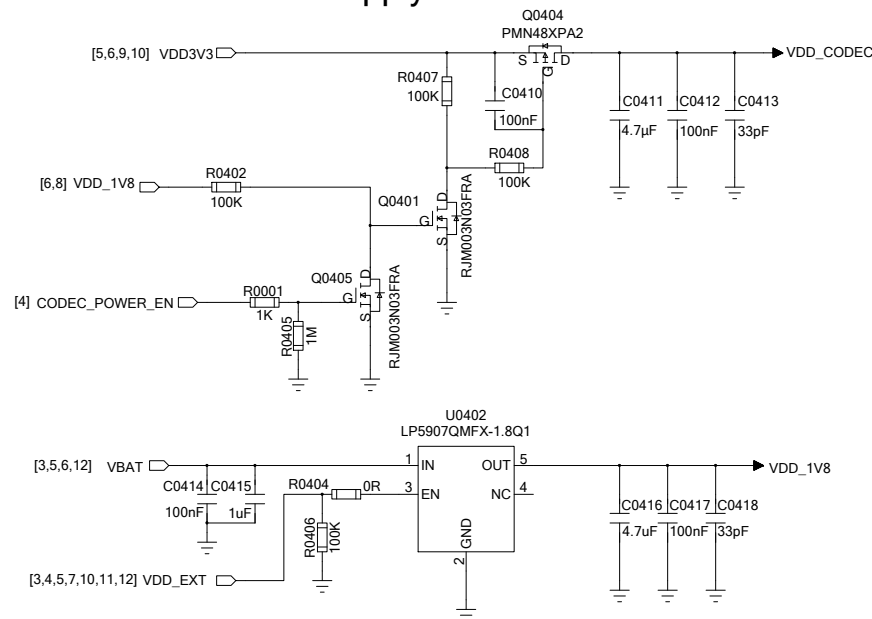

### Note:


CODEC\_POWER\_EN must be at low level to ensure normal operation of PCM codec. If VDD\_CODEC power supply needs to be switched off, keep CODEC\_POWER\_EN at high level.

### Quectel Wireless Solutions


DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 6 OF 13		DATE 2021/5/31

# (U)SIM and UART Interfaces Design

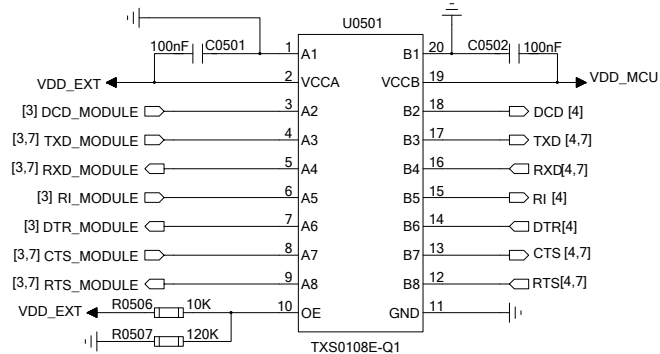
## UART Level-shifting Circuit - IC Solution (Recommended)



## (U)SIM Interface

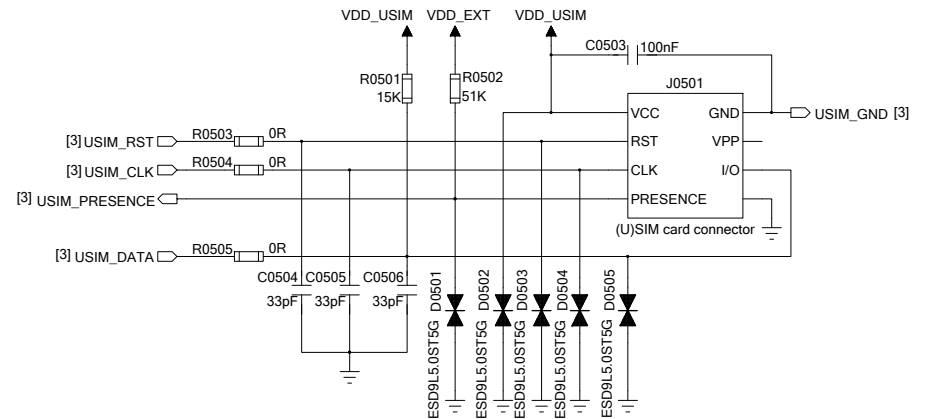
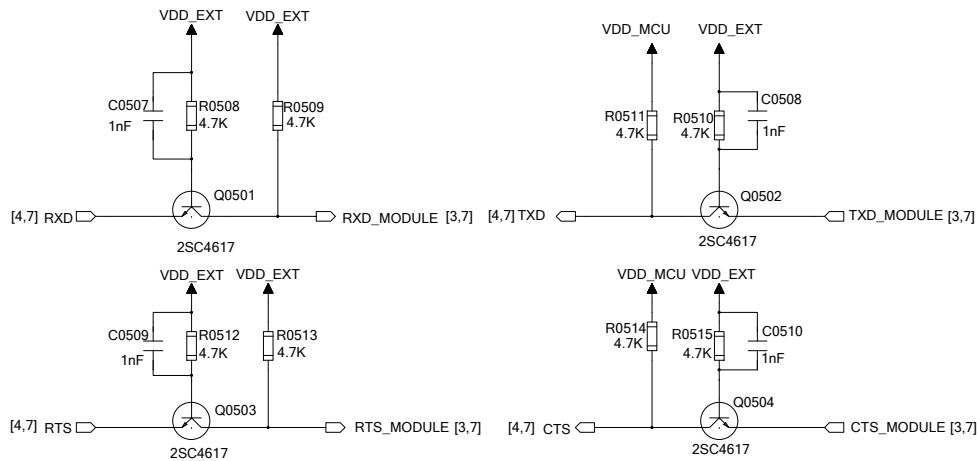
## UART Level-shifting Circuit - Transistor Solution



### Notes:

1. The decoupling capacitor of VDD\_USIM should be less than 1  $\mu$ F and must be near to (U)SIM card connector.
2. AG35 series module provides an input pin (USIM\_PRESENCE) to detect the (U)SIM card. It supports both low level and high level detection. For more details, see *Quectel\_AG35\_Hardware\_Design*.
3. R0503-R0505 are applied to suppress the EMI spurious transmission and enhance the ESD protection.
4. It is recommended to take electrostatic discharge (ESD) protection measures near the (U)SIM card connector. The TVS diode with junction capacitance less than 10 pF must be placed as close to the (U)SIM card connector as possible.
5. R0501 can improve anti-jamming capability of the (U)SIM interface circuit and it should be placed close to the (U)SIM card connector.


### Notes:

1. It is recommended to use the IC solution for voltage-level translation. The transistor solution is not suitable for applications with high baud rates exceeding 460 kbps.
2. The supply voltage range of VCCA should not exceed that of VCCB. For more information about TXS0108E-Q1, refer to the datasheet from Texas Instruments.
3. If high baud rate is needed, it is highly recommended to install four 1 nF capacitors (C0507/C0508/C0509/C0510) on transistor circuits.
4. The DTR transistor circuit is similar to that of RTS. The RI and DCD transistor circuits are similar to that of CTS.

### Quectel Wireless Solutions

DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 7 OF 13		DATE 2021/5/31


# Audio Design

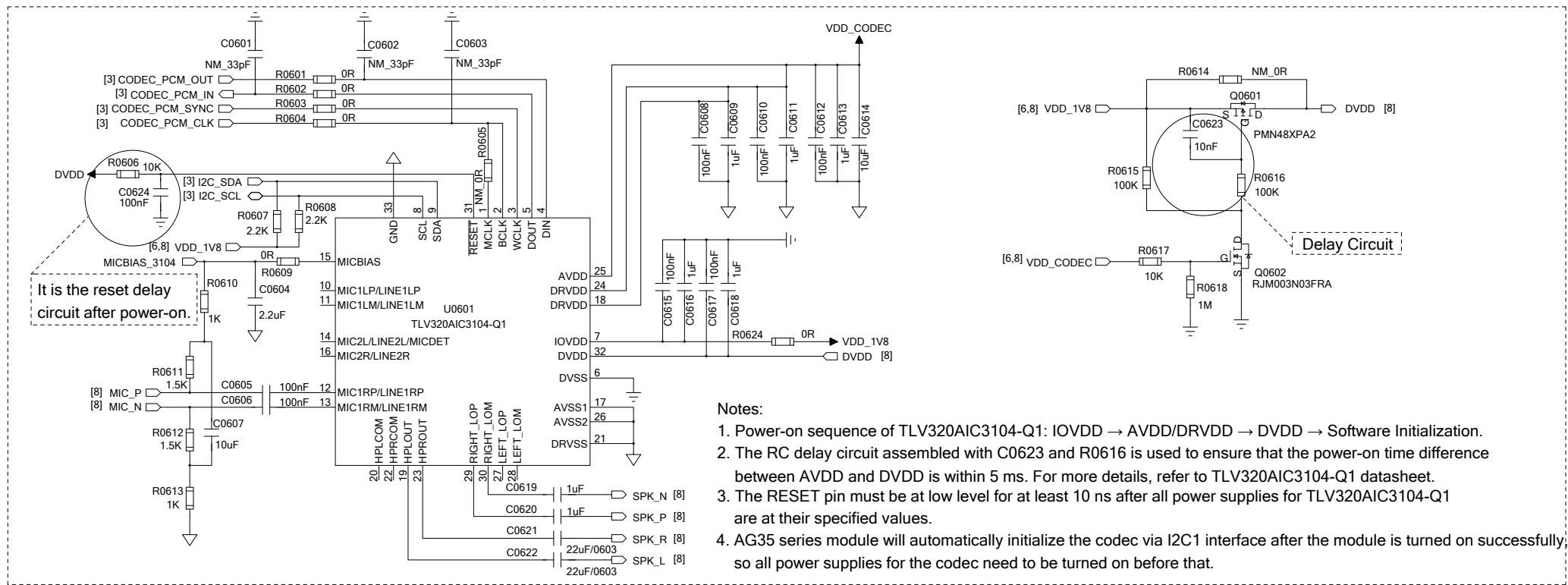

**Notes:**

1. Power-on sequence of TLV320AIC3104-Q1: IOVDD → AVDD/DRVDD → DVDD → Software Initialization.
2. The RC delay circuit assembled with C0623 and R0616 is used to ensure that the power-on time difference between AVDD and DVDD is within 5 ms. For more details, refer to TLV320AIC3104-Q1 datasheet.
3. The RESET pin must be at low level for at least 10 ns after all power supplies for TLV320AIC3104-Q1 are at their specified values.
4. AG35 series module will automatically initialize the codec via I2C1 interface after the module is turned on successfully, so all power supplies for the codec need to be turned on before that.


## Audio - Headset Application

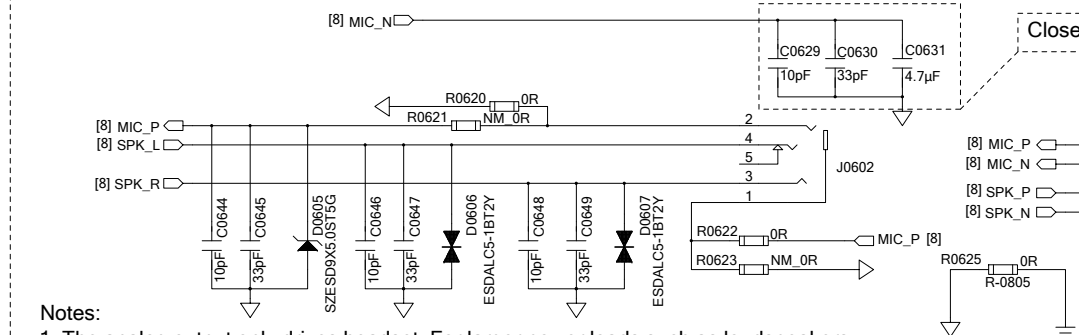

**Notes:**

1. The analog output only drives headset. For larger power loads such as loudspeakers, an audio power amplifier should be added in the circuit design.
2. The analog GND should be connected to the main GND via the 0 Ω resistor (R0625).
3. The maximum capacitive load of SPK\_N/P for speaker is 330 pF and the maximum capacitive load of MIC\_N/P for microphone is 250 pF.
4. U0602 is a simplified loudspeaker output circuit of an external power amplifier. To suppress POP, it is recommended to control the external power amplifier through PA\_EN, enabling it to be turned on after the module's audio function is established.

## Audio - Loudspeaker Application

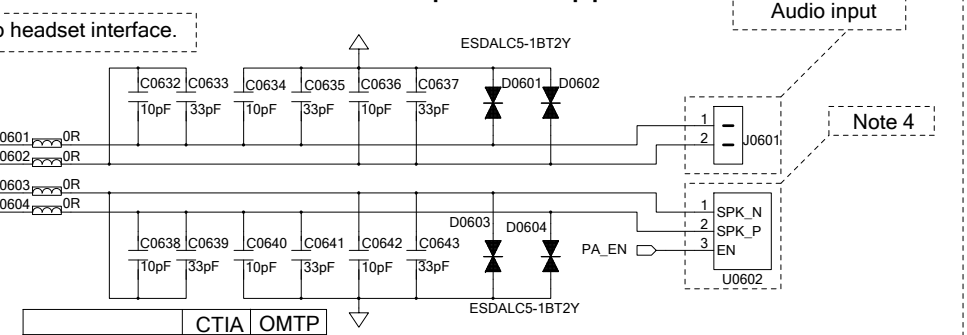


	CTIA	OMTP
R0621/R0623	NM	M
R0620/R0622	M	NM

**Quectel Wireless Solutions**

DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 8 OF 13		DATE 2021/5/31


# Antenna Interface and Antenna Detection Circuit Design
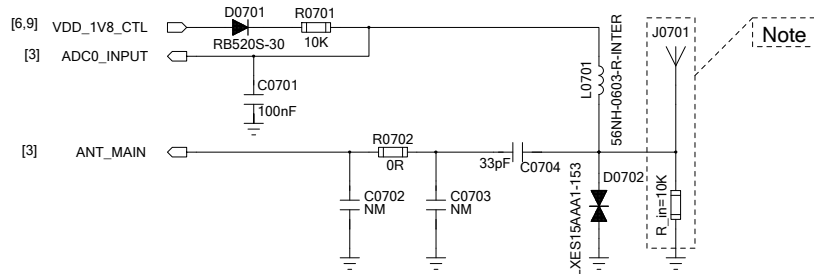
## Main Antenna Interface and Detection Circuit (Normal)



**Note:**  
To detect antenna status successfully, the main antenna is recommended to integrate an 8-13 kΩ resistor (R\_in) to GND. And the typical value for the resistor is 10 kΩ.
 
## Rx-diversity Antenna Interface and Detection Circuit (Normal)




- Notes:**
- To detect antenna status successfully, the Rx-diversity antenna is recommended to integrate an 8-13 kΩ resistor (R\_in) to GND. And the typical value for the resistor is 10 kΩ.
  - The Rx-diversity reception function is ON by default. If Rx-diversity antenna is not used, use AT command to turn off Rx-diversity reception.

Main/Rx-diversity Antenna Status Indication

Antenna Status	Open	R_in = 8 kΩ	R_in = 10 kΩ	R_in = 13 kΩ	Short to GND
ADC Value	1.7 V	0.7 V	0.8 V	0.9 V	0 V
Status Indication	Open	Normal	Normal	Normal	Short to GND

- Notes:**
- It is recommended to use n type main/Rx-diversity antenna circuit to facilitate future debugging.
  - The impedance of the RF signal traces must be controlled as 50 Ω when routing.
  - ADC value can be read by AT+QADC=<port>. For more details, see *Quectel AG35 AT Commands Manual*.
  - Three kinds of antenna status are designed to be detected: Normal, Short to GND and Open.
  - The antenna connection status is judged by the voltage detected on the ADC pins.
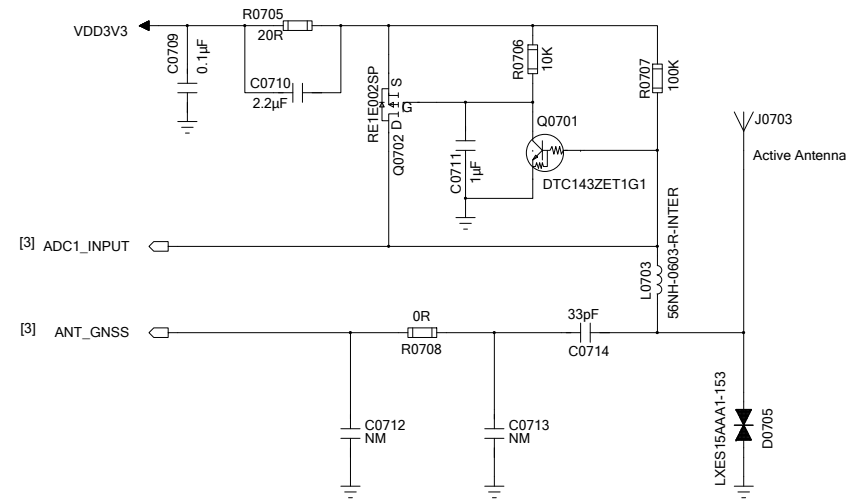
## GNSS Antenna Interface and Detection Circuit (Normal)



GNSS Antenna Status Indication

Antenna Status	Open	Normal	Short to GND
ADC Value	VDD3V3	$VDD3V3 - R0705 \times I\_GNSS$	0 V


- Notes:**
- It is recommended to select a low power active antenna.
  - An external LDO can be selected to supply power according to the active antenna requirement.
  - VDD3V3 is the power supply for active antenna, and I\_GNSS is the operating current of active antenna.
  - The active antenna power supply shall not exceed VBAT voltage of the module. And ADC0 or ADC1 shall be selected for ADC value detection.

## Quectel Wireless Solutions

DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 9 OF 13		DATE 2021/5/31



# SD Card Interface Design

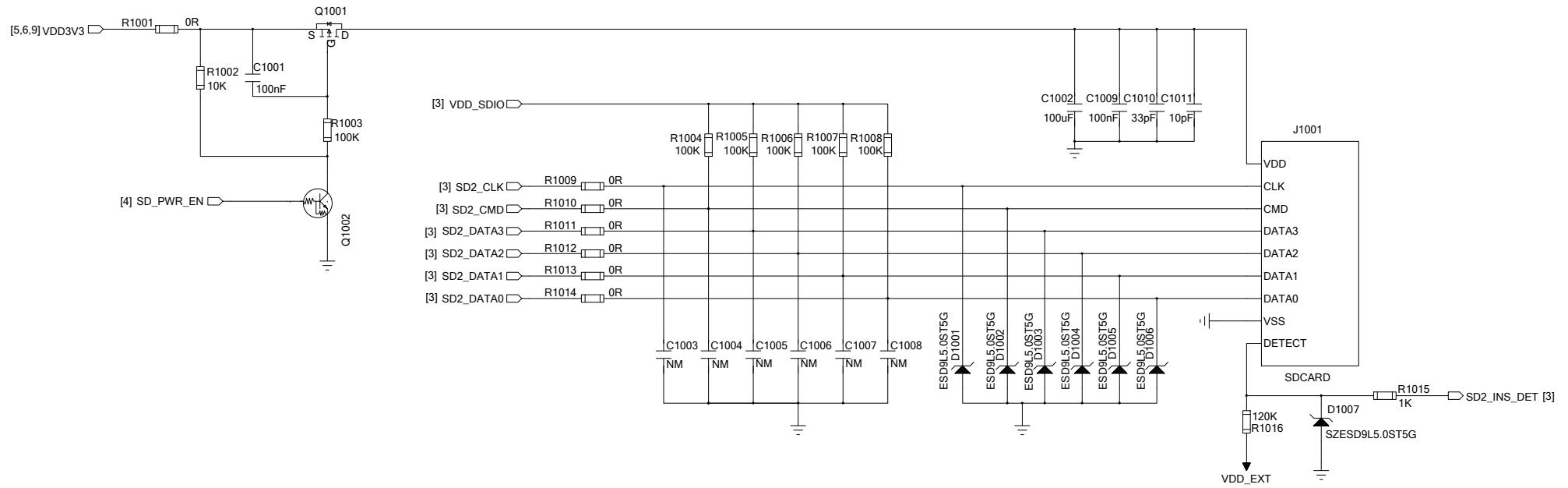

## Notes:




- VDD\_SDIO can only be used for SDIO pull-up resistors and its maximum output current is 50 mA.
- The supply voltage range of VDD for SD card interface is 2.7-3.6 V and sufficient current up to 0.8 A should be provided.
- To avoid jitter of bus, resistors R1004-R1008 are needed to pull up the SDIO to VDD\_SDIO. The value of these resistors is among 10-100 kΩ and the recommended value is 100 kΩ.
- To improve signal quality, it is recommended to add 0 Ω resistors R1009-R1014 in series between the module and the SD card connector. The bypass capacitors C1003-C1008 are reserved and not mounted by default. All resistors and bypass capacitors should be placed close to the module.
- It is recommended to add ESD protection devices near the pins of SD card connector. The parasitic capacitance of ESD protection devices should be smaller than 2 pF.
- Keep SDIO signals far away from other sensitive circuits/signals such as RF circuits and analog signals, as well as noisy signals such as clock signals and DC-DC signals.
- Route SD card signal traces with 50 Ω impedance, and it is important to route the SDIO signal traces with total grounding.
- Make sure the adjacent trace spacing is two times of the trace width and the bus capacitance is less than 40 pF.
- It is recommended to keep the trace length difference between CLK and DATA/CMD less than 1 mm. The total trace length inside the module is 23 mm, so the exterior total trace length should be less than 27 mm.
- The pin DETECT of SD card connector must be connected to the module when SD card function is used.

## Quectel Wireless Solutions

DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET	10 OF 13	DATE 2021/5/31

# AF20 Design

## AF20 Antenna Circuit

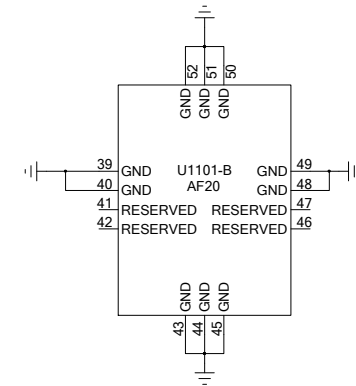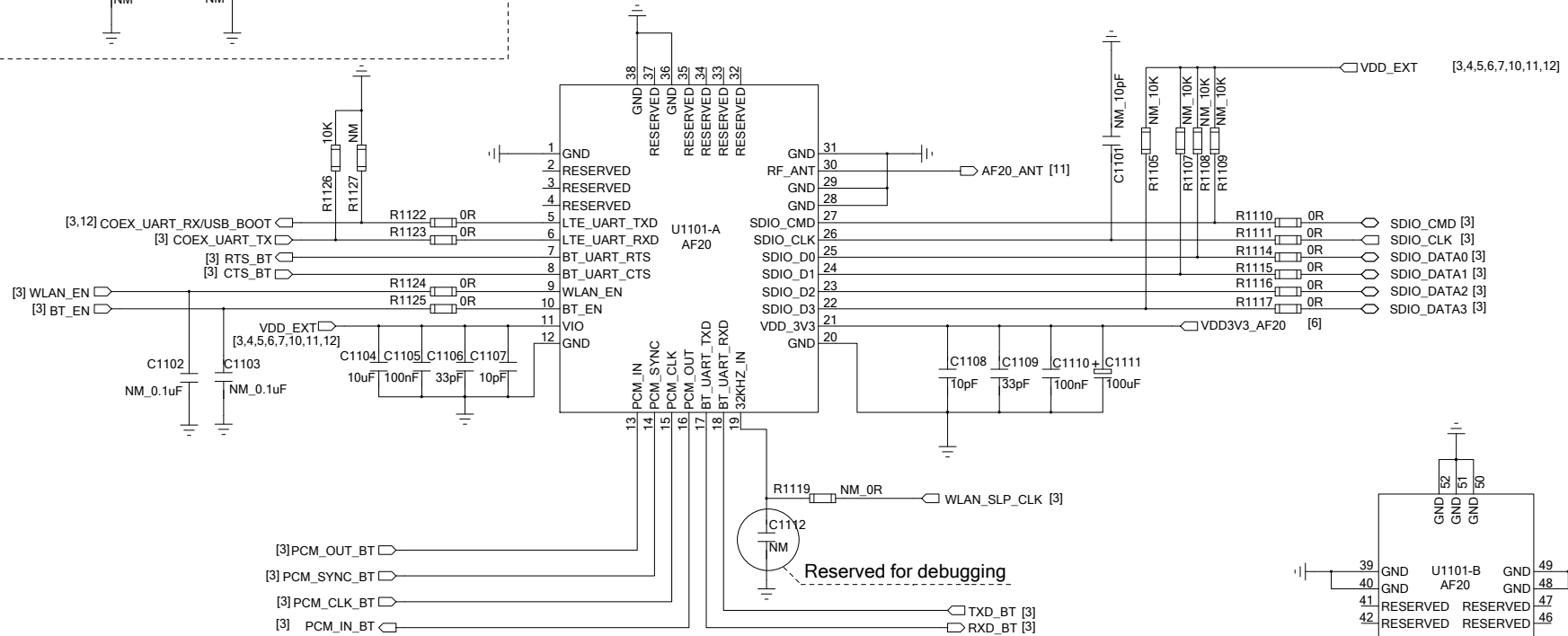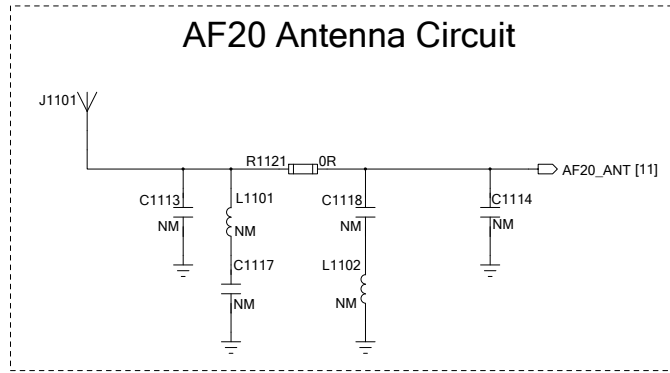

### Notes:


1. Keep all RESERVED and unused pins unconnected.
2. The impedance of the SDIO data signal traces must be controlled as 50 Ω when routing.
3. SDIO data traces should be surrounded by ground; SDIO\_CMD and SDIO\_CLK signal traces should be surrounded by ground separately.
4. It is recommended to use n type circuit for AF20 antenna design for future debugging purpose.
5. The impedance of RF signal trace must be controlled as 50 Ω when routing.

### Quectel Wireless Solutions

DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 11	OF 13	DATE 2021/5/31

# Indicators and Test Points Designs


## Indicators

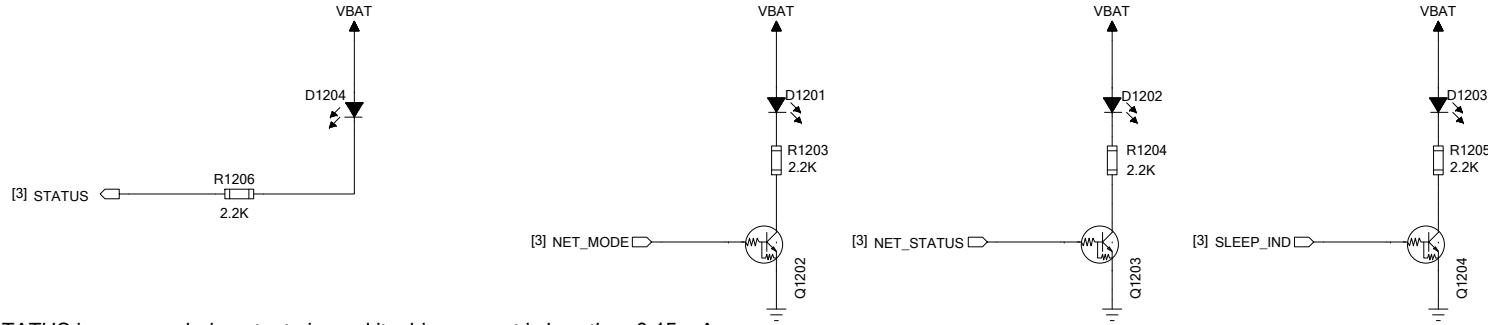

### Notes:

1. The STATUS is an open drain output pin, and its drive current is less than 0.15 mA.
2. For more details about NET\_MODE and NET\_STATUS, see *Quectel\_AG35\_Hardware\_Design*.
3. If minimized power consumption is required when the device is in sleep mode, it is recommended to replace the power supply of indicators with a controllable one, and use it to turn off the power supply when the module enters sleep mode.


## Reserved Test Points

 

### Notes:

1. Reserve the test points of USB and debug UART interfaces for software debugging.
2. USB interface also can be used to upgrade firmware.
3. Keep USB test points as close as possible to USB pins.  
Pay attention to the junction capacitance of ESD protection devices on USB data traces, which might influence the signal. Typically, the capacitance value should be less than 2 pF.
4. Debug UART interfaces support 1.8 V power domain.  
A voltage-level translator should be used if the power domain of your application is 3.3 V.

## USB\_BOOT for Download

 



### Note:

COEX\_UART\_RX/USB\_BOOT is kept open by default and the module will be forced into emergency download mode when COEX\_UART\_RX/USB\_BOOT is at high level during module power-up.

## Quectel Wireless Solutions

DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 12 OF 13	DATE 2021/5/31	

# USB Interface Design

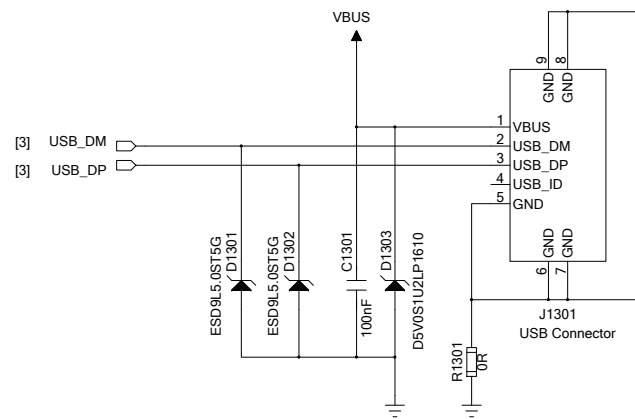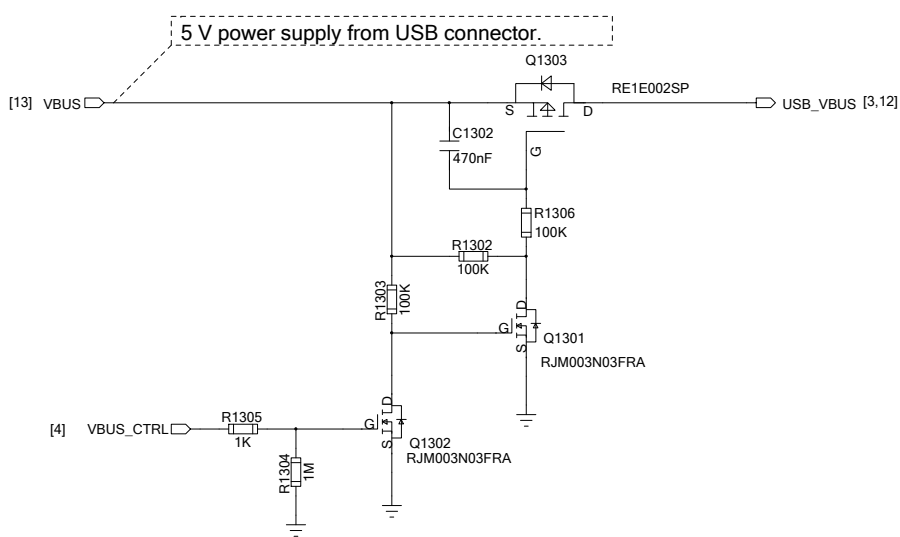

## Notes:

1. The USB\_VBUS pin of AG35 series should be powered by a 5 V power system for USB detection.
2. USB interface can be used for debugging and firmware upgrading.
3. Pay attention to the junction capacitance of ESD protection devices on USB data traces, which might influence the signal. Typically, the value of capacitance should be less than 2 pF.
4. USB\_VBUS should be controlled by USB host.

VBUS\_CTRL controlled by MCU is used to turn on/off USB\_VBUS power supply.

VBUS\_CTRL is at low level by default. When it is at high level, USB\_VBUS will be switched off.

## Quectel Wireless Solutions

DRAWN BY Eden LIU	PROJECT AG35 Series	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.1
SHEET 13 OF 13		DATE 2021/5/31